

Instituto Politécnico Nacional
Escuela Superior de Cómputo



Arquitectura de Computadoras

Practica 12: Cartas ASM

Nombre: Sampayo Hernández Mauro

Grupo: 3CV8

Profesor: Nayeli Vega García

Fecha de entrega: 18 de abril del 2020

Elementos de la Arquitectura

Código de Implementación

- Unidad de Control

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity UnidadControl is
    Port ( clk, clr, INI, z, A0 : in STD_LOGIC;
          LA, LB, EA, EB, EC : out STD_LOGIC);
end UnidadControl;
```

```
Architecture Behavioral of UnidadControl is
```

```
type estados is (e0, e1, e2);
signal edo_act, edo_sig : estados;
```

```
begin
```

```
    process (clk, clr)
    begin
        if (clr = '1') then
            edo_act <= e0;
        elsif (rising_edge(clk)) then
            edo_act <= edo_sig;
        end if;
    end process;
```

```
    process (edo_act, INI, z, A0)
    begin
        LA <= '0';
        EA <= '0';
        LB <= '0';
        EB <= '0';
        EC <= '0';

        case edo_act is
            when e0 =>--Estado 0
                LB <= '1';

                if (INI = '1') then
                    edo_sig <= e1;
                else
                    LA <= '1';
                    edo_sig <= e0;
                end if;
            when e1 =>--Estado 1
                EA <= '1';

                if (z = '1') then
                    edo_sig <= e2;
                else
                    if (A0 = '1') then
                        EB <= '1';
                    end if;
                end if;
            end case;
        end process;
```

```

        edo_sig <= e1;
    end if;
when e2 =>--Estado 2
    EC <= '1';

    if (INI = '1') then
        edo_sig <= e2;
    else
        edo_sig <= e0;
    end if;
end case;
end process;
end Behavioral;

```

- Arreglo

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Arreglo is
    Port ( EA, LA, clk, clr : in STD_LOGIC;
          DA : in STD_LOGIC_VECTOR (8 downto 0);
          QA : out STD_LOGIC_VECTOR (8 downto 0));
end Arreglo;

```

```

Architecture Behavioral of Arreglo is
begin
    process (clr, clk)
        variable arr : std_logic_vector(8 downto 0);
    begin
        if (clr = '1') then
            arr := (others => '0');
        elsif (rising_edge(clk)) then
            if LA = '1' then
                arr := DA;
            elsif EA = '1' then
                for i in 0 to 8 loop
                    if (i > 7) then
                        arr(i) := '0';
                    else
                        arr(i) := arr(i+1);
                    end if;
                end loop;
            end if;
        end if;

        QA <= arr;
    end process;
end Behavioral;

```

- Contador

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

use IEEE.STD_LOGIC_arith.ALL;
use IEEE.STD_LOGIC_unsigned.all;

entity Contador is
    Port ( clk, clr, LB, EB : in  STD_LOGIC;
          QB : out  STD_LOGIC_VECTOR (3 downto 0));
end Contador;

Architecture Behavioral of Contador is
begin
    process (clk, clr)
        variable DB : STD_LOGIC_VECTOR (3 downto 0);
    begin
        if (clr = '1') then
            DB := "0000";
        elsif (rising_edge(clk)) then
            if LB = '1' then
                DB := "0000";
            elsif EB = '1' then
                DB := DB + 1;
            end if;
        end if;

        QB <= DB;
    end process;
end Behavioral;

```

- Decodificador

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decodificador is
    Port ( QB : in  STD_LOGIC_VECTOR (3 downto 0);
          deco : out  STD_LOGIC_VECTOR(6 downto 0));
end Decodificador;

Architecture Behavioral of Decodificador is

    constant d0: STD_LOGIC_VECTOR := "0000001";
    constant d1: STD_LOGIC_VECTOR := "1001111";
    constant d2: STD_LOGIC_VECTOR := "0010010";
    constant d3: STD_LOGIC_VECTOR := "0000110";
    constant d4: STD_LOGIC_VECTOR := "1001100";
    constant d5: STD_LOGIC_VECTOR := "0100100";
    constant d6: STD_LOGIC_VECTOR := "0100000";
    constant d7: STD_LOGIC_VECTOR := "0001111";
    constant d8: STD_LOGIC_VECTOR := "0000000";
    constant d9: STD_LOGIC_VECTOR := "0000100";
    constant di: STD_LOGIC_VECTOR := "0110110"; --ERROR

begin
    deco <= d0 when QB = x"0" else
            d1 when QB = x"1" else
            d2 when QB = x"2" else
            d3 when QB = x"3" else

```

```

        d4 when QB = x"4" else
        d5 when QB = x"5" else
        d6 when QB = x"6" else
        d7 when QB = x"7" else
        d8 when QB = x"8" else
        d9 when QB = x"9" else
        di;
end Behavioral;

```

- **Multiplexor**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux is
    Port ( deco : in  STD_LOGIC_VECTOR (6 downto 0);
          OP: in STD_LOGIC;
          Q : out  STD_LOGIC_VECTOR (6 downto 0));
end Mux;

Architecture Behavioral of Mux is
begin
    Q <= deco when OP = '1' else "1111110";--guion "-"
end Behavioral;

```

- **Bandera Z**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity BanderaZ is
    Port ( Cz : in  STD_LOGIC_VECTOR (8 downto 0);
          z : out  STD_LOGIC);
end BanderaZ;

Architecture Behavioral of BanderaZ is
begin
    z <= NOT(Cz(8) OR Cz(7) OR Cz(6) OR Cz(5) OR Cz(4) OR Cz(3) OR Cz(2)
OR Cz(1) OR Cz(0));
end Behavioral;

```

Código de Simulación

- **Unidad de Control**

```

signal A0 : STD_LOGIC := '0';
signal z : STD_LOGIC := '0';

--Outputs
signal LA : STD_LOGIC;
signal LB : STD_LOGIC;
signal EA : STD_LOGIC;
signal EB : STD_LOGIC;
signal EC : STD_LOGIC;

```

```

-- Clock period definitions
constant CLK_period : time := 10 ns;

begin
-- Instantiate the Unit Under Test (UUT)
 uut: UnidadControl
    Port Map ( clk => clk,
               clr => clr,
               INI => INI,
               A0 => A0,
               z  => z,
               LB => LB,
               LA => LA,
               EA => EA,
               EB => EB,
               EC => EC);

-- Clock process definitions
CLK_process :process
begin
    clk <= '0';
    wait for CLK_period/2;
    clk <= '1';
    wait for CLK_period/2;
end process;

-- Stimulus process
stim_proc: process
begin
    clr <= '1';
    wait for 30 ns;
    clr <= '0';
    wait for 10 ns;
    --estado 0 -> estado 1
    INI <= '1';
    A0 <= '1';
    z <= '0';
    wait for 50 ns;
    --estado 1 -> estado 2
    INI <= '1';
    A0 <= '0';
    z <= '1';
    wait for 50 ns;
    --estado 2 -> estado 0
    INI <= '0';
    wait for 50 ns;
    wait;
end process;
end Behavioral;

```

- Arreglo

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

```

```
entity Arreglo_tb is
end Arreglo_tb;
```

```
Architecture Behavioral of Arreglo_tb is
```

```
    component Arreglo is
        Port ( EA, LA, clk, clr : in  STD_LOGIC;
              DA : in  STD_LOGIC_VECTOR (8 downto 0);
              QA : out STD_LOGIC_VECTOR (8 downto 0));
    end component;
```

```
--Inputs
```

```
signal clk : STD_LOGIC := '0';
signal clr : STD_LOGIC := '0';
signal EA : STD_LOGIC := '0';
signal LA : STD_LOGIC := '0';
signal DA : STD_LOGIC_VECTOR (8 downto 0) := (others => '1');
```

```
--Outputs
```

```
signal QA : STD_LOGIC_VECTOR(8 downto 0);
```

```
-- Clock period definitions
```

```
constant CLK_period : time := 10 ns;
```

```
begin
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
ut: Arreglo
    Port Map ( clk => clk,
               clr => clr,
               EA => EA,
               LA => LA,
               DA => DA,
               QA => QA);
```

```
-- Clock process definitions
```

```
CLK_process :process
```

```
begin
```

```
    clk <= '0';
    wait for CLK_period/2;
    clk <= '1';
    wait for CLK_period/2;
end process;
```

```
-- Stimulus process
```

```
stim_proc: process
```

```
begin
```

```
    LA <= '1';
    wait for 10 ns;
    LA <= '0';
    wait for 10 ns;
    clr <= '1';
    wait for 10 ns;
    clr <= '0';
    wait for 10 ns;
    LA <= '1';
    wait for 10 ns;
    LA <= '0';
```

```

        wait for 10 ns;
        EA <= '1';
        wait for 30 ns;
        EA <= '0';
        wait for 10 ns;
        EA <= '1';
        wait for 30 ns;
        EA <= '0';
        wait for 10 ns;
        wait;
    end process;
end Behavioral;

```

- Contador

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

```

```

entity Contador_tb is
end Contador_tb;

```

```

Architecture Behavioral of Contador_tb is

```

```

    component Contador is
        Port ( clk, clr, LB, EB : in STD_LOGIC;
              QB : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

```

```

--Inputs

```

```

signal clk : STD_LOGIC := '0';
signal clr : STD_LOGIC := '0';
signal LB : STD_LOGIC := '0';
signal EB : STD_LOGIC := '0';

```

```

--Outputs

```

```

signal QB : STD_LOGIC_VECTOR(3 downto 0);

```

```

-- Clock period definitions

```

```

constant CLK_period : time := 10 ns;

```

```

begin

```

```

    -- Instantiate the Unit Under Test (UUT)

```

```

    uut: Contador

```

```

        Port Map ( clk => clk,
                   clr => clr,
                   LB => LB,
                   EB => EB,
                   QB => QB);

```

```

    -- Clock process definitions

```

```

    CLK_process :process

```

```

    begin

```

```

        clk <= '0';
        wait for CLK_period/2;
        clk <= '1';
        wait for CLK_period/2;

```



```


end process;

-- Stimulus process
stim_proc: process
begin
    clr <= '1';
    wait for 30 ns;
    clr <= '0';
    wait for 30 ns;
    LB <= '0';
    EB <= '1';
    wait for 100 ns;
    EB <= '1';
    wait for 100 ns;
    EB <= '0';
    LB <= '1';
    wait for 100 ns;
    clr <= '1';
    wait for 30 ns;
    clr <= '0';
    wait;
end process;
end Behavioral;


```

Simulación:

- Unidad de Control

 

- Arreglo

 

- Contador



 


Diagrama RTL:


- Unidad de Control

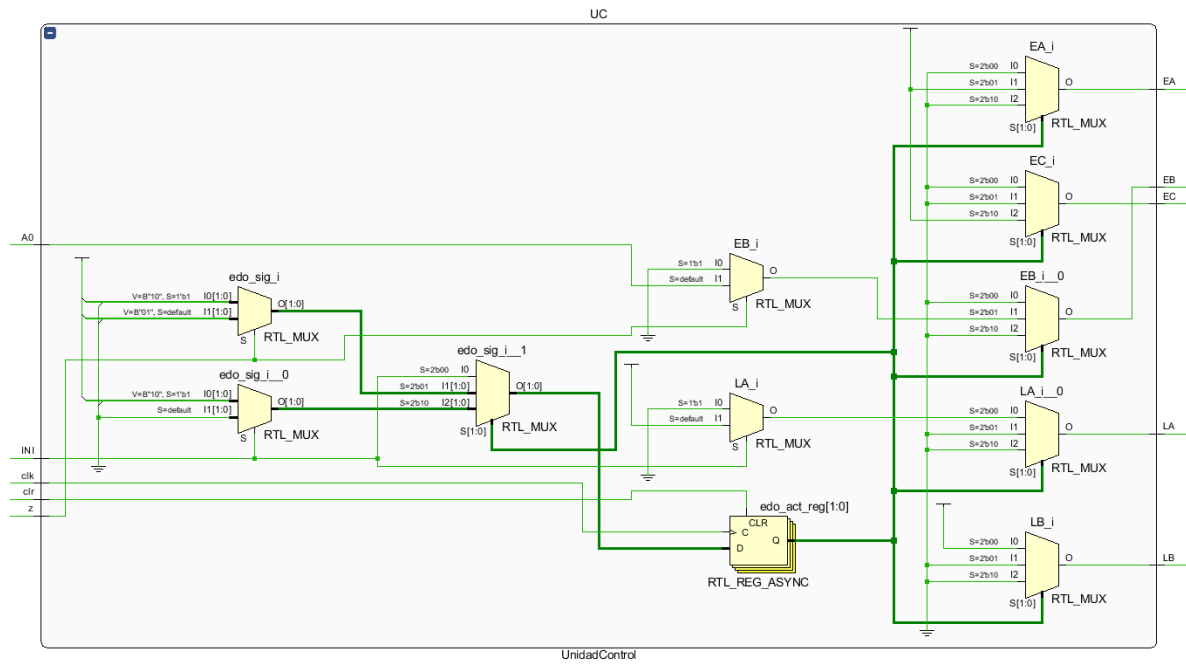


- Arreglo

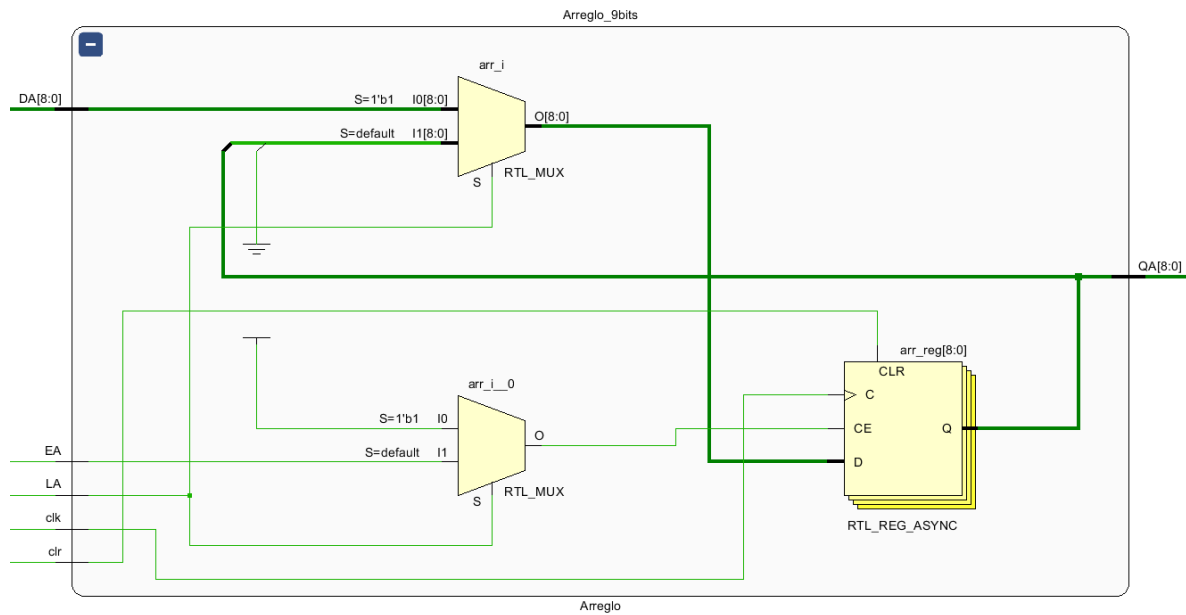


- Contador

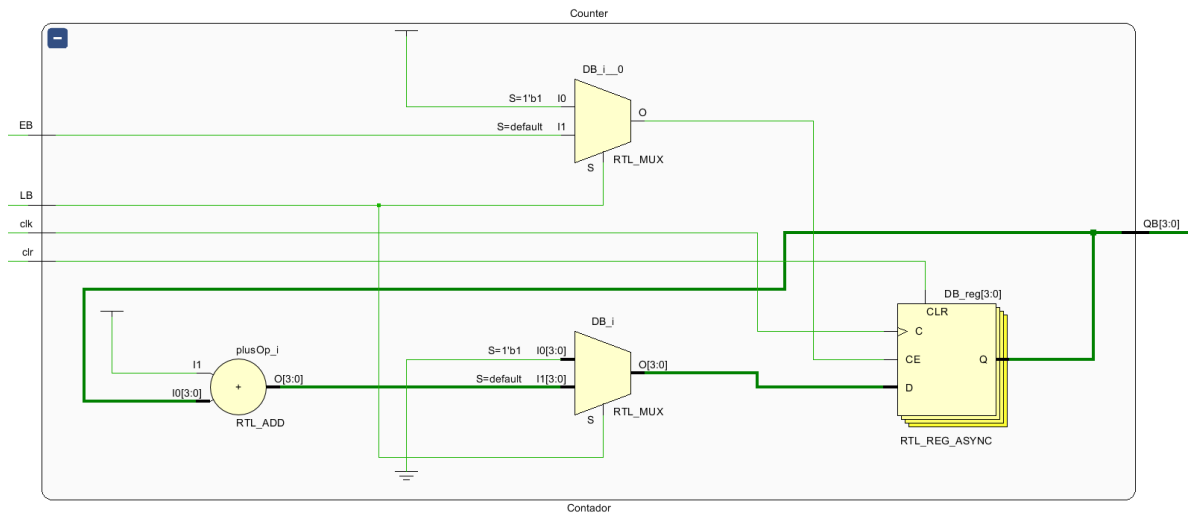


- Decodificador

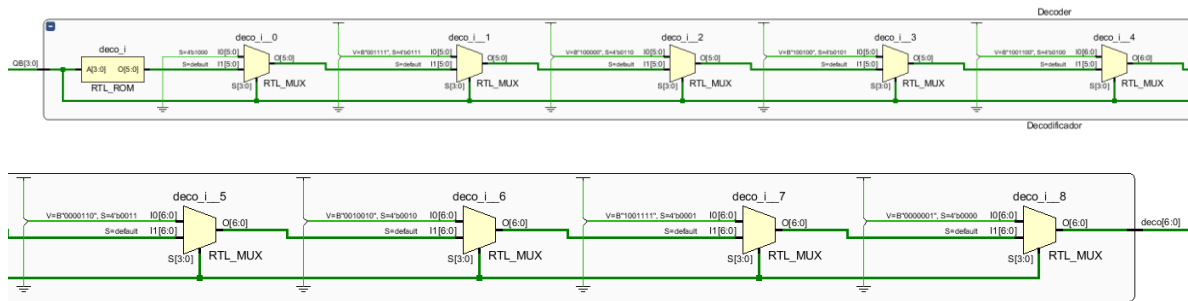

- Multiplexor

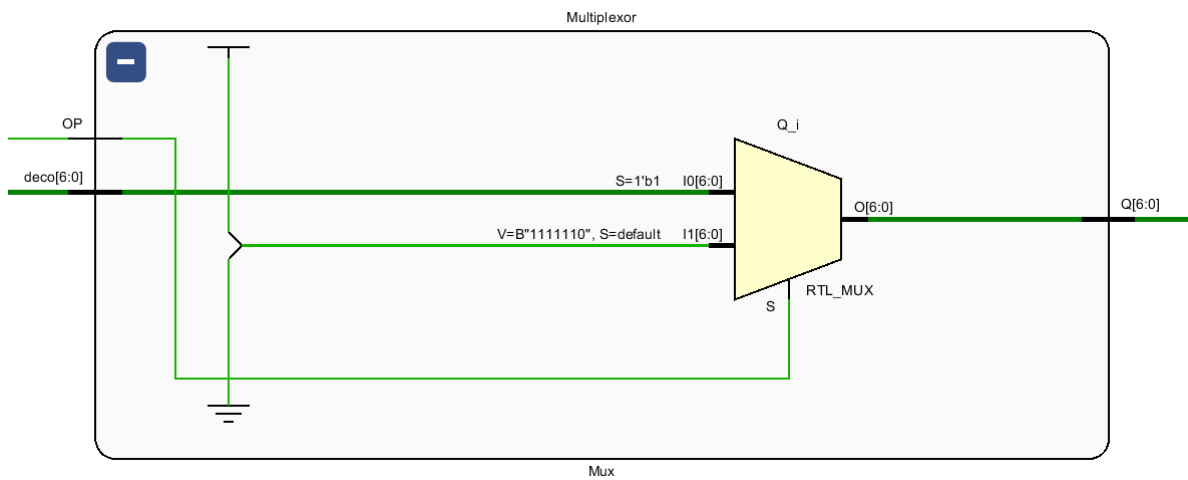

- **Bandera Z**

 

Arquitectura Completa

Código de Implementación

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity cartaASM is
    Port ( INI, clk, clr : in  STD_LOGIC;
          D : in  STD_LOGIC_VECTOR (8 downto 0);
          A : out STD_LOGIC_VECTOR (8 downto 0); --Salida Arreglo
          B : out STD_LOGIC_VECTOR (6 downto 0)); --Salida Display (Mux)
end cartaASM;

Architecture Behavioral of cartaASM is

    component Arreglo is
        Port ( EA, LA, clk, clr : in  STD_LOGIC;
              DA : in  STD_LOGIC_VECTOR (8 downto 0);
              QA : out  STD_LOGIC_VECTOR (8 downto 0));
    end component;

    component Contador is
        Port ( clk, clr, LB, EB : in  STD_LOGIC;
              QB : out  STD_LOGIC_VECTOR (3 downto 0));
    end component;

    component Decodificador is
        Port ( QB : in  STD_LOGIC_VECTOR (3 downto 0);
              deco : out  STD_LOGIC_VECTOR (6 downto 0));
    end component;

    component Mux is
        Port ( deco : in  STD_LOGIC_VECTOR (6 downto 0);
              OP: in  STD_LOGIC;
              Q : out  STD_LOGIC_VECTOR (6 downto 0));
    end component;

    component UnidadControl is
        Port ( clk, clr, INI, z, A0 : in  STD_LOGIC;
              LA, LB, EA, EB, EC : out STD_LOGIC);
    end component;

    component BanderaZ is
        Port ( Cz : in  STD_LOGIC_VECTOR (8 downto 0);
              z : out  STD_LOGIC);
    end component;
```

```

    signal A0, z, LA, LB, EA, EB, EC: STD_LOGIC;
    signal B1: STD_LOGIC_VECTOR(3 DOWNTO 0);
    signal Cz: STD_LOGIC_VECTOR(8 downto 0);
    signal B_aux: STD_LOGIC_VECTOR(6 downto 0);--auxiliar de la salida
del Dsiplay(B) para evitar corto circuito uwu

begin
    A <= Cz;
    A0 <= Cz(0);

    Bandera_Z : BanderaZ
        Port map( Cz => Cz,
            z => z);

    UC : UnidadControl
        Port Map( clk => clk,
            clr => clr,
            INI => INI,
            A0 => A0,
            z => z,
            LA => LA,-- A=D
            LB => LB,-- B=0
            EA => EA,-- A>>1
            EB => EB,-- B++
            EC => EC);-- Mostrar B

    Counter : Contador
        Port Map( clk => clk,
            clr => clr,
            LB => LB,
            EB => EB,
            QB => B1);

    Arreglo_9bits : Arreglo
        Port MAP( clk => clk,
            clr => clr,
            DA => D,
            EA => EA,
            LA => LA,
            QA => Cz);

    Decoder: Decodificador
        Port Map( QB => B1,
            deco => B_aux);

    Multiplexor: Mux
        Port Map( deco => B_aux,
            OP => EC,
            Q => B);
end Behavioral;

```

Código de Simulación

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

```

```

entity cartaASM_tb is
end cartaASM_tb;

Architecture Behavioral of cartaASM_tb is

    component cartaASM is
        Port ( INI, clk, clr : in  STD_LOGIC;
              D : in  STD_LOGIC_VECTOR (8 downto 0);
              A : out STD_LOGIC_VECTOR (8 downto 0);
              B : out STD_LOGIC_VECTOR (6 downto 0));
    end component;

    --Inputs
    signal clk : STD_LOGIC := '0';
    signal clr : STD_LOGIC := '0';
    signal INI : STD_LOGIC := '0';
    signal D : STD_LOGIC_VECTOR(8 downto 0) := (others => '0');

    --Outputs
    signal A : STD_LOGIC_VECTOR(8 downto 0);
    signal B : STD_LOGIC_VECTOR(6 downto 0);

    -- Clock period definitions
    constant CLK_period : time := 10 ns;

begin
    -- Instantiate the Unit Under Test (UUT)
    uut: cartaASM
        Port Map ( clk => clk,
                   clr => clr,
                   INI => INI,
                   D => D,
                   A => A,
                   B => B);

    -- Clock process definitions
    CLK_process :process
    begin
        clk <= '0';
        wait for CLK_period/2;
        clk <= '1';
        wait for CLK_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        clr <= '1';
        wait for 10 ns;
        clr <= '0';
        d <= "101101011";-- inciso a
        wait for 50 ns;
        ini <= '1';
        wait for 150 ns;
        ini <= '0';
        d <= "000011101";--inciso b
    end process;
end Behavioral;

```

```

wait for 50 ns;
ini <= '1';
wait for 150 ns;
ini <= '0';
d <= "000010000";--inciso c
wait for 50 ns;
ini <= '1';
wait for 150 ns;
ini <= '0';
d <= "100001000";--inciso d
wait for 50 ns;
ini <= '1';
wait for 150 ns;
ini <= '0';
d <= "000000000";--inciso e
wait for 50 ns;
wait;
end process;
end Behavioral;

```

Simulación:

 


Diagrama RTL:

